



Need:

- ① momentary pushbutton or switch
- ② 4.7K resistor
- ③ 3-conductor wire

Solder the 3 wires to 2 tabs.

Connect 3 wires to input card

In DMX with CIO-DIO24, pins

35 & 36 are response button input.

pin 21 = GND

pin 20 = +5V